

VLSI: Switch-Level and Gate-Level System Design

Tassadaq Hussain


Namal University Mianwali

PakASIC.com

Outline


Verilog
Modelsim

Behavioral
level of
abstraction

 


BEHAVIORAL D.

STRUCTURAL D.

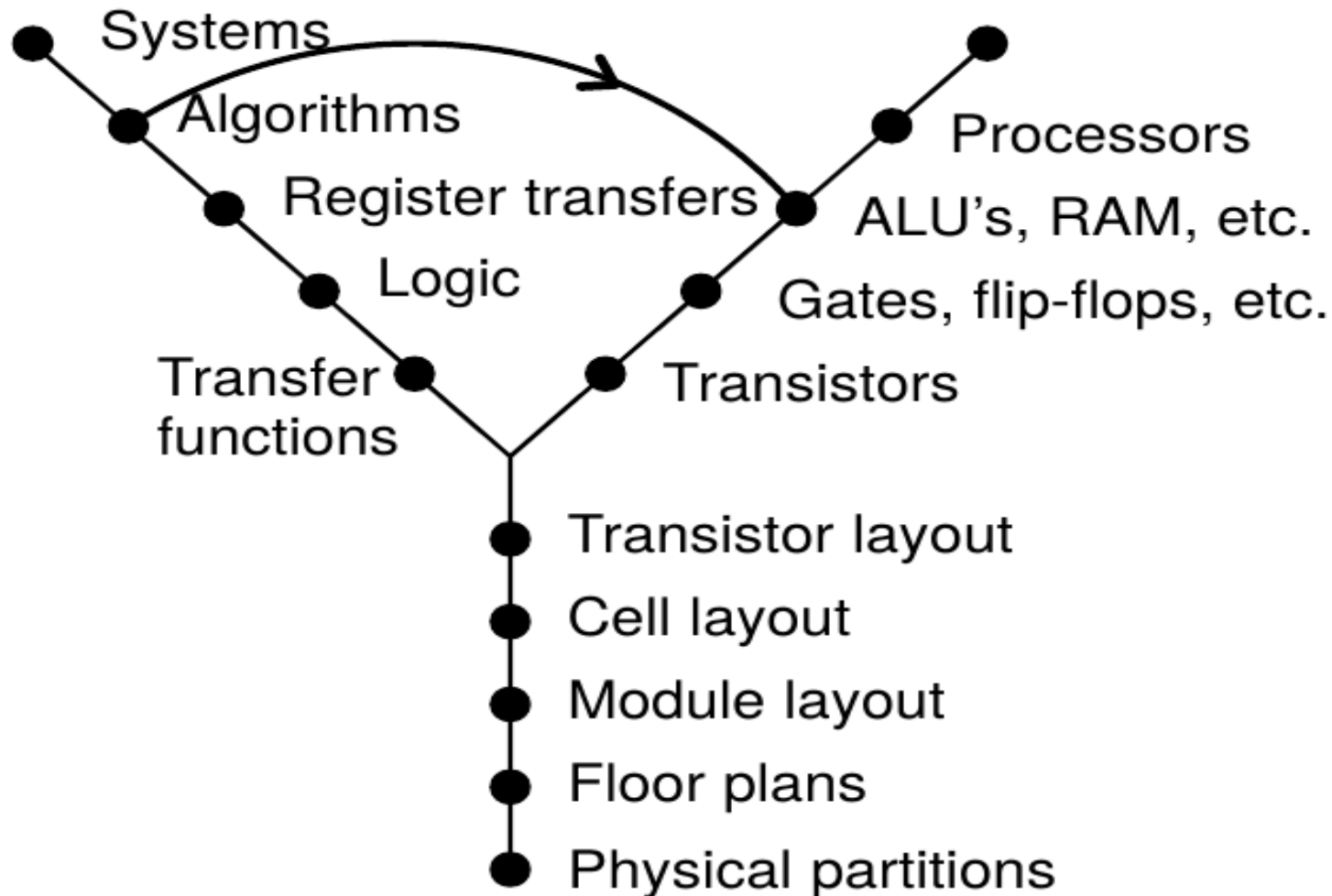

PHYSICAL D.

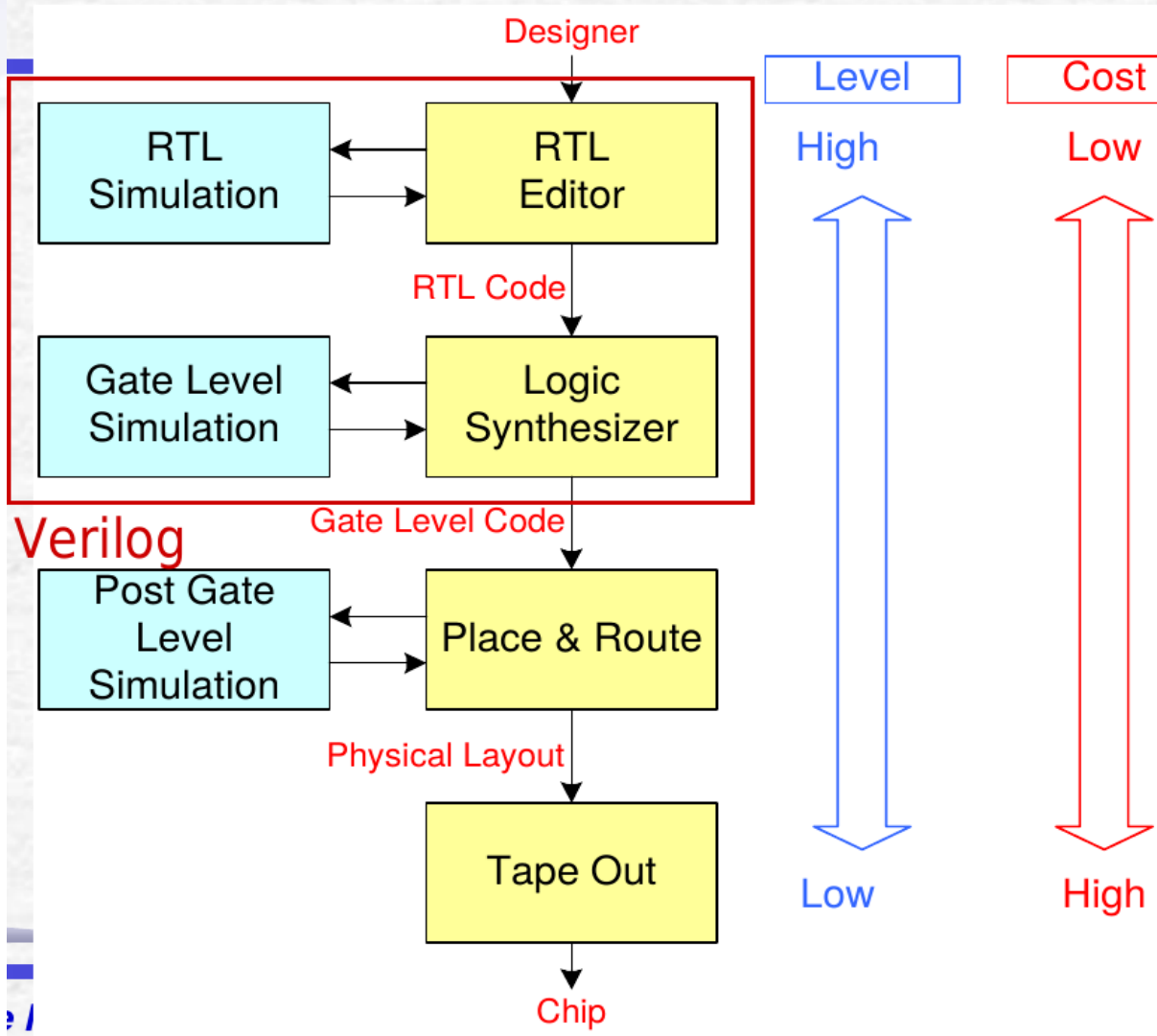



Verilog HDL Switch Level

- Verilog provides the ability to design at a MOS-transistor level.
- Design at switch level is becoming rare with the increasing complexity of circuits (millions of transistors) and with the availability of sophisticated CAD tools.
- Verilog HDL currently provides only digital design capability with logic values 0, 1, X, z, and the drive strengths associated with them.
- There is no analog capability. Thus, in Verilog HDL, transistors are also known switches that either conduct or are open.

Objectives

- Describe basic MOS switches nmos, pmos, and cmos.
- Understand modeling of bidirectional pass switches, power, and ground.
- Identify resistive MOS switches.
- Explain the method to specify delays on basic MOS switches and bidirectional pass switches.
- Build basic switch-level circuits in Verilog, using available switches.
  
```
//MOS switch keywords  
nmos          pmos
```




```
nmos n1(out, data, control); //instantiate a nmos switch  
pmos p1(out, data, control); //instantiate a pmos switch
```

Logic Tables for NMOS and PMOS

		control			
		0	1	x	z
data	0	z	0	L	L
	1	z	1	H	H
	x	z	x	x	x
	z	z	z	z	z




		control			
		0	1	x	z
data	0	0	z	L	L
	1	1	z	H	H
	x	x	z	x	x
	z	z	z	z	z

CMOS Switch

 

```
cmos c1(out, data, ncontrol, pcontrol); //instantiate cmos gate.  
or  
cmos (out, data, ncontrol, pcontrol); //no instance name given.
```

Bidirectional Switches

   

```
tran t1(inout1, inout2); //instance name t1 is optional  
tranif0 (inout1, inout2, control); //instance name is not specified  
tranif1 (inout1, inout2, control); //instance name is not specified
```

Power and Ground

```
supply1 vdd;  
supply0 gnd;
```

```
assign a = vdd; //Connect a to vdd  
assign b = gnd; //Connect b to gnd
```

Delays

Switch Element	Delay Specification	Examples
pmos, nmos, rpmos, rnmos	Zero (no delay) One (same delay on all transitions) Two (rise, fall) Three (rise, fall, turnoff)	pmos p1(out, data, control); pmos #(1) p1(out, data, control); nmos #(1, 2) p2(out, data, control); nmos #(1, 3, 2) p2(out, data, control);
cmos, rcmos	Zero, one, two or three delays (same as above)	cmos #(5) c2(out, data, nctrl, pctrl); cmos #(1,2) c1(out, data, nctrl, pctrl);


Switch Element	Delay Specification	Examples
tran, rtran	No delay specification allowed	
tranif1, rtranif1 tranif0, rtranif0	Zero (no delay) One (both turn-on and turn-off) Two (turn-on, turn-off)	rtranif0 rt1(inout1, inout2, control); tranif0 #(3) T(inout1, inout2, control); tranif1 #(1,2) t1(inout1, inout2, control);

Example

CMOS NOR Gate

```
//Define our own nor gate, m_nor
```


 
```
module my_nor (out, a, b);  
output out;  
input a, b;  
//internal wires  
wire c;  
//set up power and ground lines  
supply1 pwr;  
//pwr is connected to Vdd (power supply)  
supply0 gnd;  
//gnd is connected to Vss(ground)  
//instantiate pmos switches  
pmos (c, pwr, b);  
pmos (out, c, a);  
//instantiate nmos switches  
nmos (out, gnd, a);  
nmos (out, gnd, b);  
endmodule
```



Test bench

```
//stimulus to test the gate
module stimulus;
reg A, B;
wire OUT;
//instantiate the my_nor module
my_nor n1(OUT, A, B);
//Apply stimulus
initial
begin
//test all possible combinations
A=1'b0; B = 1'b0;
#5 A=1'b0; B=1'b1;
#5 A=1'b1; B=1'b0;
#5 A=1'b1; B=1'b1;
end
//check results
initial
$monitor("Time", $time, " OUT %b, A %b, B %b", OUT, A, B);
endmodule
```


2 to 1 Mux

  


Objectives: Gate Level Design

- Identify logic gate primitives provided in Verilog.
- Understand instantiation of gates, gate symbols and truth tables for and/or and buf/not type gates.
- Understand how to construct a Verilog description from the logic diagram of the circuit.
- Describe rise, fall, and turn-off delays in the gate-level design.
- Explain min, max, and type delays in the gate-level design.


Gate Level Modeling

 


and

 

nand

 


or

 

nor



xor

 


xnor

and
nand

or
nor

xor
xnor

 

www.asic-world.com

Basic Gates Instantiation

```
and a1(OUT, IN1, IN2);  
nand na1(OUT, IN1, IN2);  
or or1(OUT, IN1, IN2);  
nor nor1(OUT, IN1, IN2);  
xor x1(OUT, IN1, IN2);  
xnor nx1(OUT, IN1, IN2);
```

Types of Gates

And/Or Gates


Buff/Not

And/Or Gates


and
nand

or
nor

xor
xnor

 


and

 

nand




or

 

nor



xor

 

xnor

Basic Gates

```
// basic gate instantiations.  
and a1(OUT, IN1, IN2);  
nand na1(OUT, IN1, IN2);  
or or1(OUT, IN1, IN2);  
nor nor1(OUT, IN1, IN2);  
xor x1(OUT, IN1, IN2);  
xnor nx1(OUT, IN1, IN2);  
  
// More than two inputs; 3 input nand gate  
nand na1_3inp(OUT, IN1, IN2, IN3);  
  
// gate instantiation without instance name  
and (OUT, IN1, IN2); // legal gate instantiation
```

Truth Table of Gates

		i1			
		0	1	x	z
i2	and	0	0	0	0
	1	0	1	x	x
	x	0	x	x	x
	z	0	x	x	x

		i1			
		0	1	x	z
i2	nand	1	1	1	1
	1	1	0	x	x
	x	1	x	x	x
	z	1	x	x	x

		i1			
		0	1	x	z
i2	or	0	1	x	x
	1	1	1	1	1
	x	x	1	x	x
	z	x	1	x	x

		i1			
		0	1	x	z
i2	nor	1	0	x	x
	1	0	0	0	0
	x	x	0	x	x
	z	x	0	x	x





		i1			
		0	1	x	z
i2	xor	0	1	x	x
	1	1	0	x	x
	x	x	x	x	x
	z	x	x	x	x

		i1			
		0	1	x	z
i2	xnor	1	0	x	x
	1	0	1	x	x
	x	x	x	x	x
	z	x	x	x	x

Buf/Not Gates

```
// basic gate instantiations.  
buf b1(OUT1, IN);  
not n1(OUT1, IN);  
  
// More than two outputs  
buf b1_2out(OUT1, OUT2, IN);  
  
// gate instantiation without instance name  
not (OUT1, IN); // legal gate instantiation
```


Bufif / Notif

    

Bufif / Notif


```
//Instantiation of bufif gates.  
bufif1 b1 (out, in, ctrl);  
bufif0 b0 (out, in, ctrl);  
  
//Instantiation of notif gates  
notif1 n1 (out, in, ctrl);  
notif0 n0 (out, in, ctrl);
```

Example

 



s_1	s_0	out
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

Gate Level Diagram

 


4 Bit Adder

 

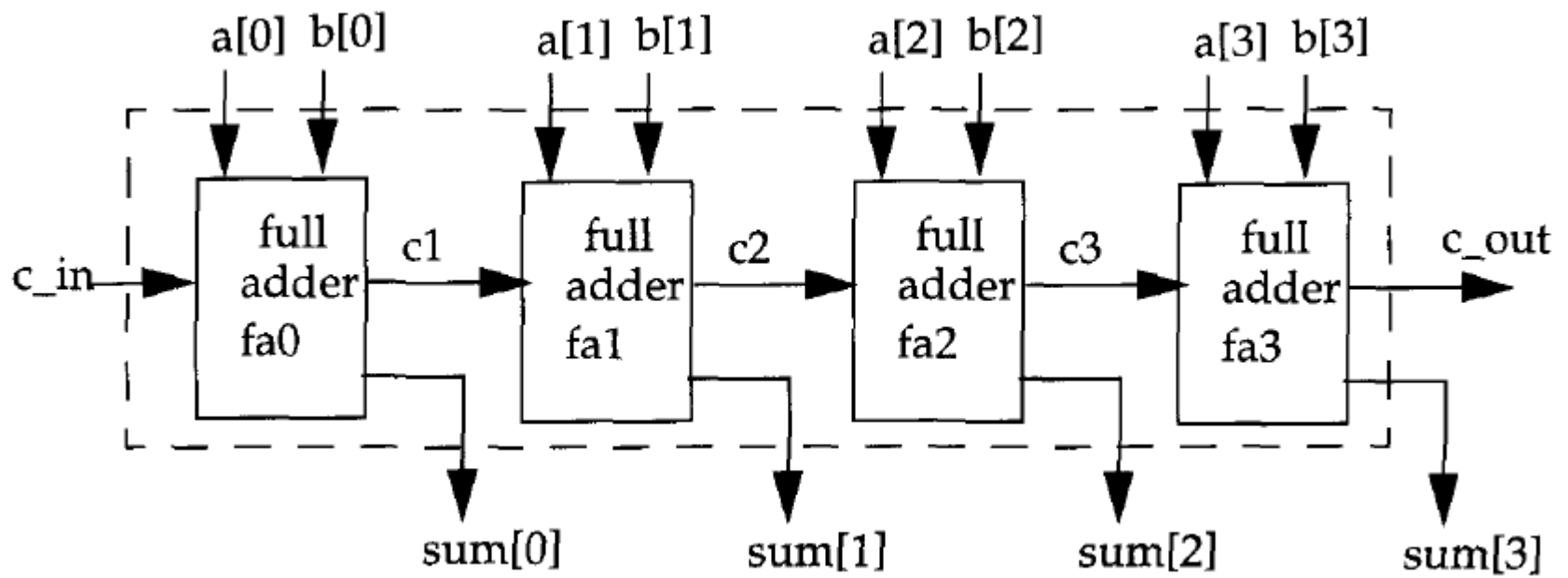

Gate Delays

Rise, Fall, and Turn-off Delays

 

Min/Typ/Max Value

```
// One delay
// if +mindelays, delay= 4
// if +typdelays, delay= 5
// if +maxdelays, delay= 6
and #(4:5:6) a1(out, i1, i2);
```

```
// Two delays
// if +mindelays, rise= 3, fall= 5, turn-off = min(3,5)
// if +typdelays, rise= 4, fall= 6, turn-off = min(4,6)
// if +maxdelays, rise= 5, fall= 7, turn-off = min(5,7)
and #(3:4:5, 5:6:7) a2(out, i1, i2);
```

```
// Three delays
// if +mindelays, rise= 2 fall= 3 turn-off = 4
// if +typdelays, rise= 3 fall= 4 turn-off = 5
// if +maxdelays, rise= 4 fall= 5 turn-off = 6
and #(2:3:4, 3:4:5, 4:5:6) a3(out, i1, i2);
```

Turn-off Delay

The Turn-off delay is associated with a gate output transition to z from another value $(0, 1, x)$.

Design Gate/Switch Level

Inverter

Comparative

Counter

Multiplexer

Adder

Logic Indicator