

Power and Energy: VLSI Design

Dr. Tassadaq Hussain
Computer Architect
Co-Founder PakAsic.com




Outline

Power and Energy

Dynamic Power

Static Power

 

Power and Energy

Power is drawn from a voltage source attached to the V_{DD} pin(s) of a chip.

Instantaneous Power:

Energy:

Average Power:

Power in Circuit Elements

$$P_{VDD}(t) = I_{DD}(t)V_{DD}$$



$$P_R(t) = \frac{V_R^2(t)}{R} = I_R^2(t)R$$



$$\begin{aligned} E_C &= \int_0^{\infty} I(t)V(t)dt = \int_0^{\infty} C \frac{dV}{dt} V(t)dt \\ &= C \int_0^{V_C} V(t)dV = \frac{1}{2} CV_C^2 \end{aligned}$$



Charging a Capacitor

When the gate output rises

Energy stored in capacitor is

$$E_C = \frac{1}{2} C_L V_{DD}^2$$

But energy drawn from the supply is


$$\begin{aligned} E_{V_{DD}} &= \int_0^{\infty} I(t) V_{DD} dt = \int_0^{\infty} C_L \frac{dV}{dt} V_{DD} dt \\ &= C_L V_{DD} \int_0^{V_{DD}} dV = C_L V_{DD}^2 \end{aligned}$$

Half the energy from V_{DD} is dissipated in the pMOS transistor as heat, other half stored in capacitor

When the gate output falls


Energy in capacitor is dumped to GND

 Dissipated as heat in the nMOS transistor



Switching Power
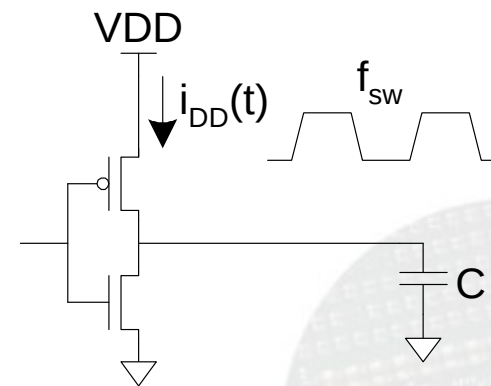
$$\begin{aligned} P_{\text{switching}} &= \frac{1}{T} \int_0^T i_{DD}(t) V_{DD} dt \\ &= \frac{V_{DD}}{T} \int_0^T i_{DD}(t) dt \\ &= \frac{V_{DD}}{T} [T f_{\text{sw}} C V_{DD}] \\ &= C V_{DD}^2 f_{\text{sw}} \end{aligned}$$



Activity Factor

Suppose the system clock frequency = f

Let $f_{sw} = \alpha f$, where α = activity factor

If the signal is a clock, $\alpha = 1$

If the signal switches once per cycle, $\alpha = 1/2$

Dynamic power: $P_{switching} = \alpha C V_{DD}^2 f$

Short Circuit Current

When transistors switch, both nMOS and pMOS networks may be momentarily ON at once

Leads to a blip of “short circuit” current.

< 10% of dynamic power if rise/fall times are comparable for input and output

We will generally ignore this component

Power Dissipation Sources

$$P_{\text{total}} = P_{\text{dynamic}} + P_{\text{static}}$$

$$\text{Dynamic power: } P_{\text{dynamic}} = P_{\text{switching}} + P_{\text{shortcircuit}}$$

Switching load capacitances

Short-circuit current

$$\text{Static power: } P_{\text{static}} = (I_{\text{sub}} + I_{\text{gate}} + I_{\text{junct}} + I_{\text{contention}})V_{\text{DD}}$$

Subthreshold leakage

Gate leakage

Junction leakage

Contention current

A digital system-on-chip in a 1 V 65 nm process (with 50 nm drawn channel lengths and $\lambda = 25$ nm) has 1 billion transistors, of which 50 million are in logic gates and the remainder in memory arrays. The average logic transistor width is 12λ and the average memory transistor width is 4λ . The memory arrays are divided into banks and only the necessary bank is activated so the memory activity factor is 0.02. The static CMOS logic gates have an average activity factor of 0.1. Assume each transistor contributes 1 fF/ μ m of gate capacitance and 0.8 fF/ μ m of diffusion capacitance. Neglect wire capacitance for now (though it could account for a large fraction of total power). Estimate the switching power when operating at 1 GHz.

Dynamic Power Example

1 billion transistor chip

50M logic transistors

- Average width: 12λ
- Activity factor = 0.1

950M memory transistors

- Average width: 4λ
- Activity factor = 0.02

1.0 V 65 nm process

$C = 1 \text{ fF}/\mu\text{m}$ (gate) + $0.8 \text{ fF}/\mu\text{m}$ (diffusion)

Estimate dynamic power consumption @ 1 GHz. Neglect wire capacitance and short-circuit current.

Solution

$$C_{\text{logic}} = (50 \times 10^6)(12\lambda)(0.025 \mu\text{m} / \lambda)(1.8 \text{ fF} / \mu\text{m}) = 27 \text{ nF}$$

$$C_{\text{mem}} = (950 \times 10^6)(4\lambda)(0.025 \mu\text{m} / \lambda)(1.8 \text{ fF} / \mu\text{m}) = 171 \text{ nF}$$

$$P_{\text{dynamic}} = \left[0.1C_{\text{logic}} + 0.02C_{\text{mem}} \right] (1.0)^2 (1.0 \text{ GHz}) = 6.1 \text{ W}$$

Dynamic Power Reduction

$$P_{\text{switching}} = \alpha C V_{DD}^2 f$$

Try to minimize:

Activity factor

Capacitance

Clock Gating

Voltage Scaling

Frequency Scaling: Dynamic Voltage and Frequency Scaling (DVFS)

Power Gating:

Multi-Voltage Design:

Data and Instruction Compression:

Pipeline Balancing:

Clock Tree Optimization

Low Power Design Methodologies


Clock Gating

The best way to reduce the activity is to turn off the clock to registers in unused blocks

Saves clock activity ($\alpha = 1$)

Eliminates all switching activity in the block

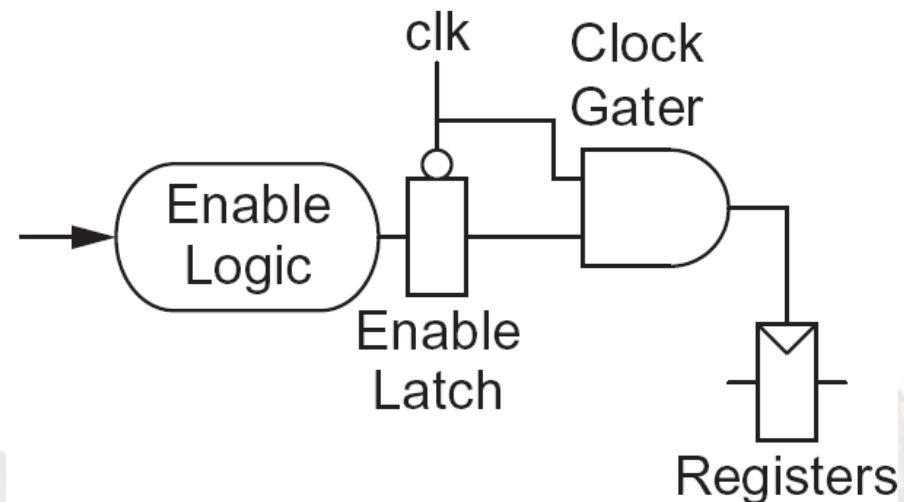Requires determining if block will be used



Capacitance

- Gate capacitance
- Fewer stages of logic
- Small gate sizes
- Wire capacitance
- Good floorplanning to keep communicating blocks close to each other
- Drive long wires with inverters or buffers rather than complex gates

Voltage / Frequency

Run each block at the lowest possible voltage and frequency that meets performance requirements



Voltage Domains

Provide separate supplies to different blocks

Level converters required when crossing
from low to high V_{DD} domains

Dynamic Voltage Scaling

  Adjust V_{DD} and f according to
workload



Static Power

Static power is consumed even when chip is quiescent.
Leakage draws power from nominally OFF devices
Ratio circuits burn power in fight between ON transistors

Leakage Control

Leakage and delay trade off

Aim for low leakage in sleep and low delay in active mode

To reduce leakage:

Increase V_t : *multiple* V_t

- Use low V_t only in critical circuits

Increase V_s : *stack effect*

- *Input vector control* in sleep

Decrease V_b

- *Reverse body bias* in sleep
- Or *forward body bias* in active mode

